
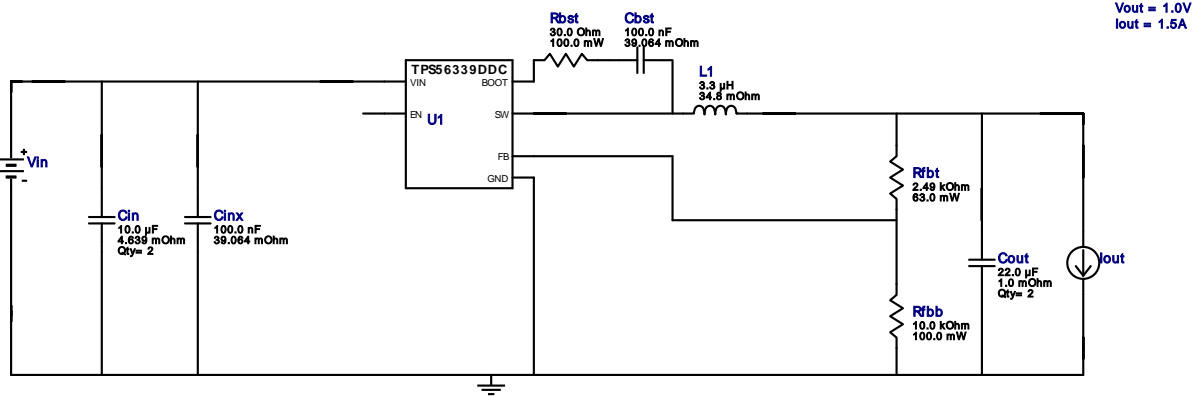
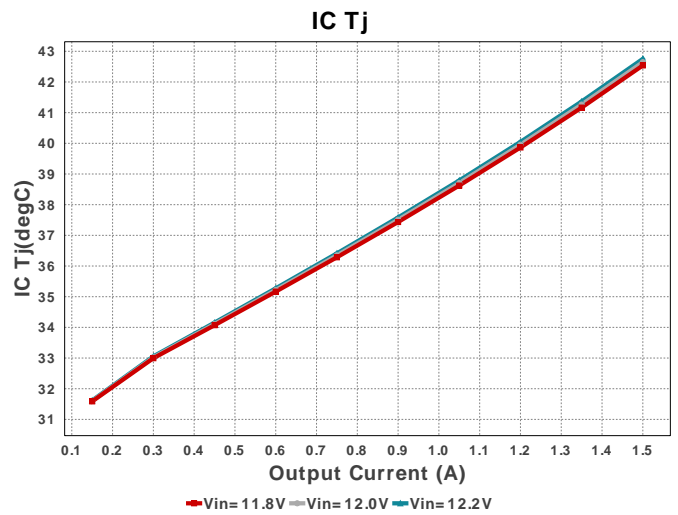
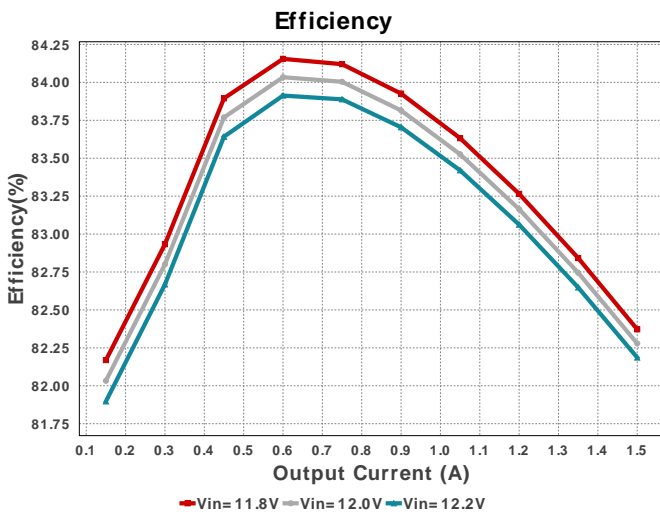
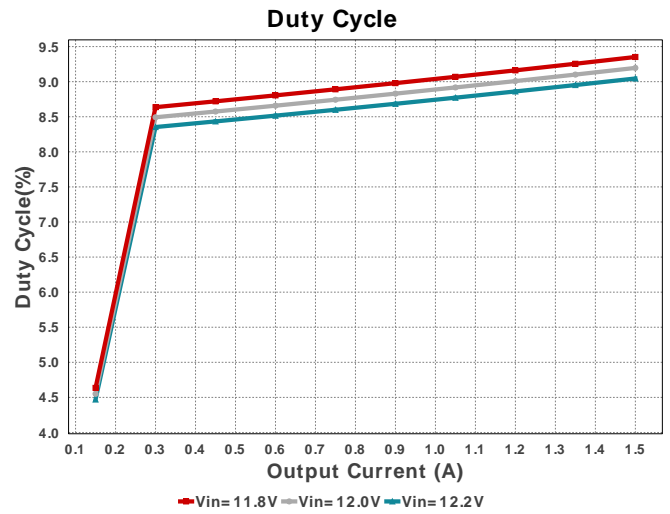
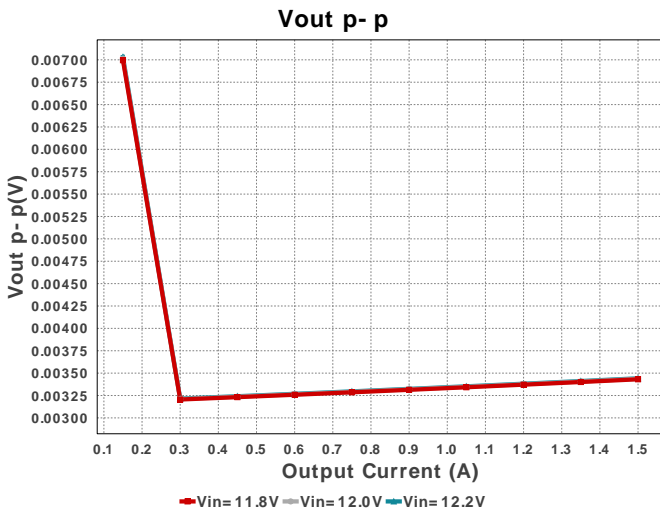
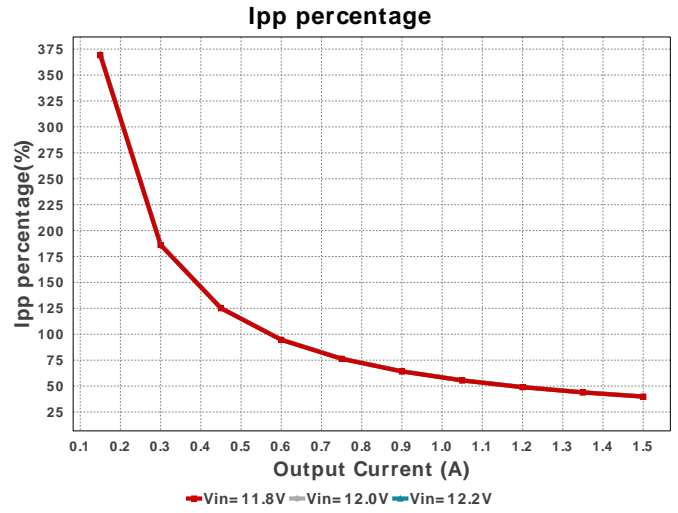
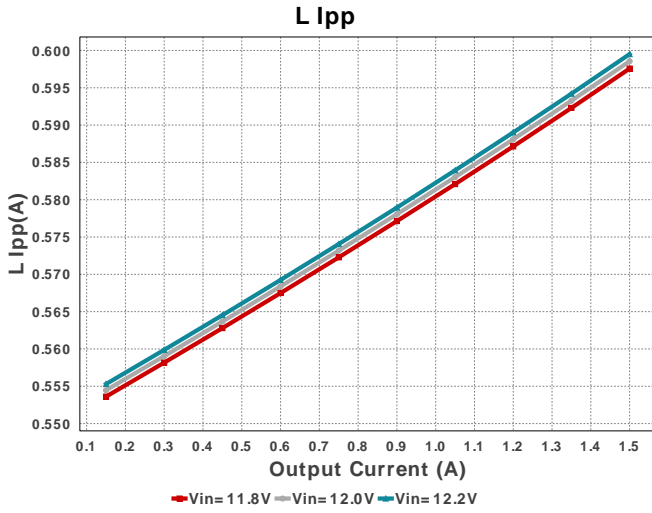
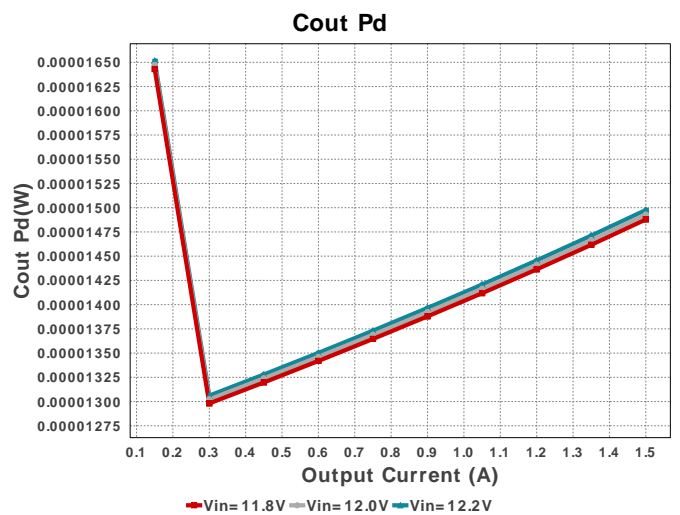
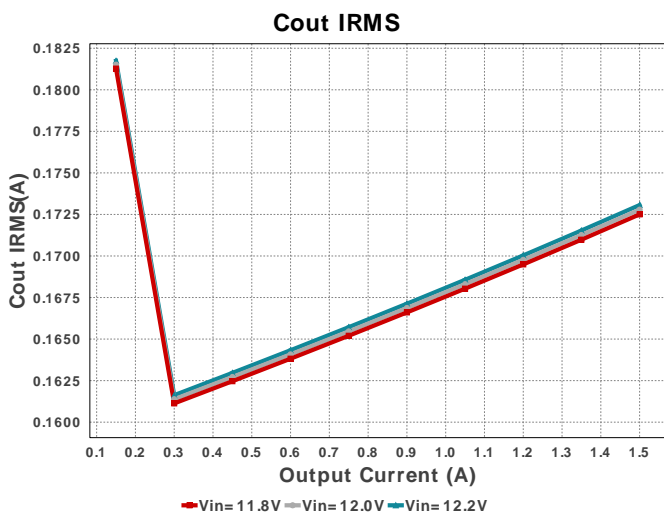
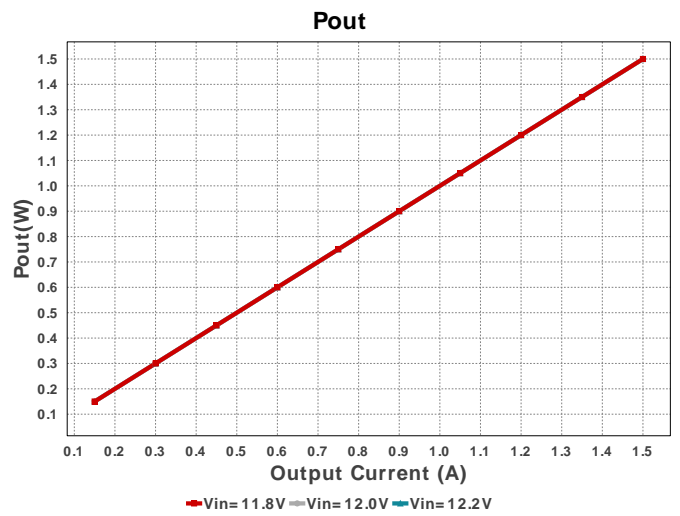
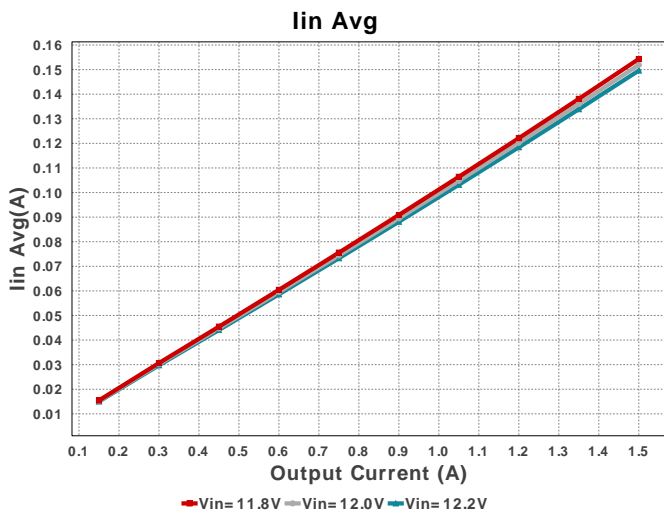
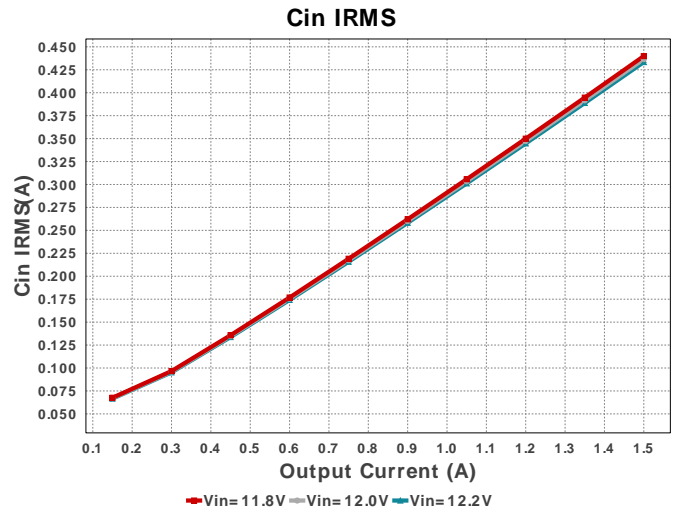



**WEBENCH® Design Report**

 Design : 7 TPS56339DDCR  
 TPS56339DDCR 11.8V-12.2V to 1.00V @ 1.5A

**Electrical BOM**

Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cbst	TDK	CGA2B3X7R1H104K050BB Series= X7R	Cap= 100.0 nF ESR= 39.064 mOhm VDC= 50.0 V IRMS= 814.67 mA	1	\$0.02	0402 3 mm <sup>2</sup>
Cin	TDK	C1608X5R1E106M080AC Series= X5R	Cap= 10.0 uF ESR= 4.639 mOhm VDC= 25.0 V IRMS= 2.4141 A	2	\$0.20	0603 5 mm <sup>2</sup>
Cinx	TDK	CGA2B3X7R1H104K050BB Series= X7R	Cap= 100.0 nF ESR= 39.064 mOhm VDC= 50.0 V IRMS= 814.67 mA	1	\$0.02	0402 3 mm <sup>2</sup>
Cout	TDK	C2012X7S1A226M125AC Series= X7S	Cap= 22.0 uF ESR= 1.0 mOhm VDC= 10.0 V IRMS= 0.0 A	2	\$0.29	0805 7 mm <sup>2</sup>
L1	Coilcraft	XFL4020-332MEB	L= 3.3 uH 34.8 mOhm	1	\$0.61	XFL4020 25 mm <sup>2</sup>
Rbst	Yageo	RC0603FR-0730RL Series= ?	Res= 30.0 Ohm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	0603 5 mm <sup>2</sup>
Rfbb	KOA Speer	RK73H1ETTP1002F Series= ?	Res= 10.0 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>
Rfbt	Vishay-Dale	CRCW04022K49FKED Series= CRCW...e3	Res= 2.49 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>
U1	Texas Instruments	TPS56339DDCR	Switcher	1	\$0.38	DDC0006A_N 10 mm <sup>2</sup>

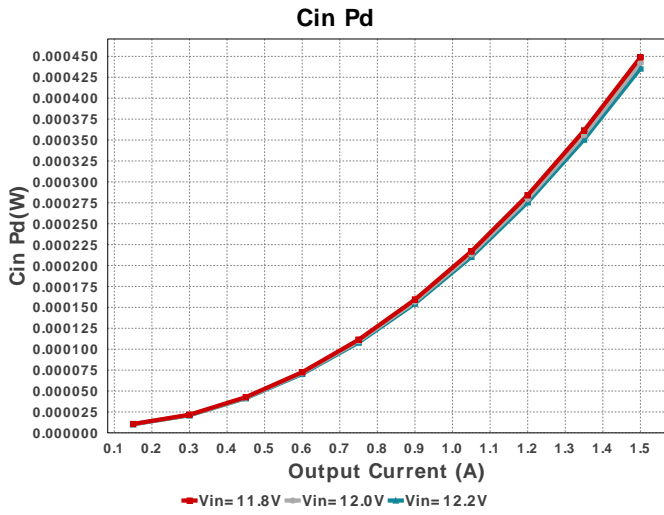

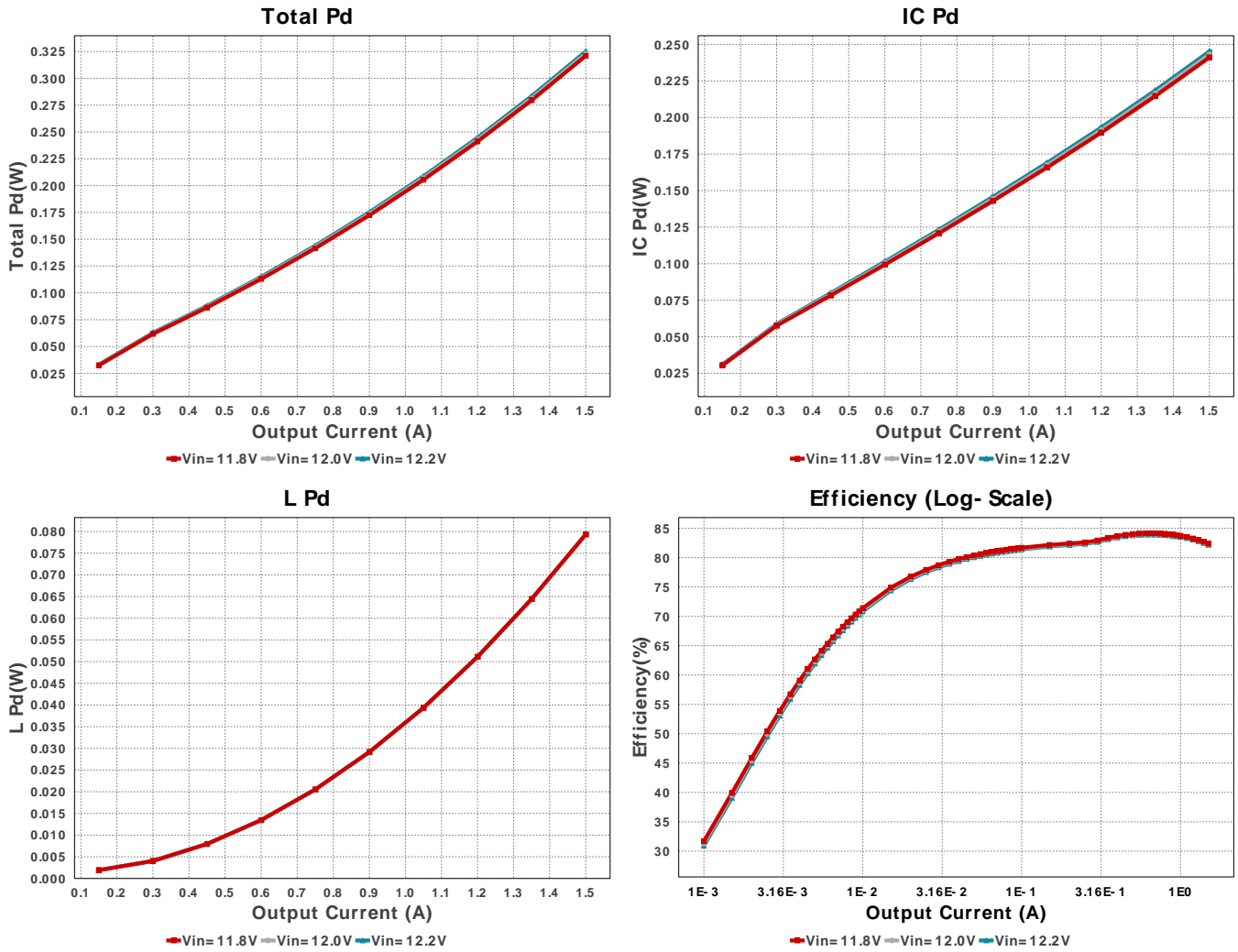



### Operating Values

#	Name	Value	Category	Description
1.	BOM Count	11		Total Design BOM count
2.	Total BOM	\$2.038		Total BOM Cost
3.	Cin IRMS	433.377 mA	Capacitor	Input capacitor RMS ripple current
4.	Cin Pd	435.64 $\mu$ W	Capacitor	Input capacitor power dissipation
5.	Cout IRMS	173.064 mA	Capacitor	Output capacitor RMS ripple current
6.	Cout Pd	14.976 $\mu$ W	Capacitor	Output capacitor power dissipation
7.	IC Pd	245.25 mW	IC	IC power dissipation
8.	IC Tj	42.753 degC	IC	IC junction temperature
9.	ICThetaJA Effective	52.0 degC/W	IC	Effective IC Junction-to-Ambient Thermal Resistance
10.	Iin Avg	149.6 mA	IC	Average input current
11.	Ipp percentage	39.967 %	Inductor	Inductor ripple current percentage (with respect to average inductor current)
12.	L Ipp	599.511 mA	Inductor	Peak-to-peak inductor ripple current
13.	L Pd	79.342 mW	Inductor	Inductor power dissipation
14.	Cin Pd	435.64 $\mu$ W	Power	Input capacitor power dissipation
15.	Cout Pd	14.976 $\mu$ W	Power	Output capacitor power dissipation
16.	IC Pd	245.25 mW	Power	IC power dissipation
17.	L Pd	79.342 mW	Power	Inductor power dissipation
18.	Total Pd	325.127 mW	Power	Total Power Dissipation
19.	Duty Cycle	9.045 %	System	Duty cycle
20.	Efficiency	82.186 %	System	Steady state efficiency
21.	FootPrint	75.0 mm <sup>2</sup>	System	Total Foot Print Area of BOM components
22.	Frequency	505.071 kHz	System	Switching frequency
23.	Iout	1.5 A	System	Iout operating point
24.	Mode	CCM	System	Conduction Mode

#	Name	Value	Category	Description
25.	Pout	1.5 W	System Information	Total output power
26.	Vin	12.2 V	System Information	Vin operating point
27.	Vout	1.0 V	System Information	Operational Output Voltage
28.	Vout Actual	999.2 mV	System Information	Vout Actual calculated based on selected voltage divider resistors
29.	Vout Tolerance	2.913 %	System Information	Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable
30.	Vout p-p	3.442 mV	System Information	Peak-to-peak output ripple voltage

## Design Inputs

Name	Value	Description
Iout	1.5	Maximum Output Current
VinMax	12.2	Maximum input voltage
VinMin	11.8	Minimum input voltage
VinTyp	12.0	Typical input voltage
Vout	1.0	Output Voltage
base_pn	TPS56339	Base Product Number
source	DC	Input Source Type
Ta	30.0	Ambient temperature

## WEBENCH® Assembly

### Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of  $C_{in}$  and  $C_{out}$ , and the inductance and DC resistance of L1 before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

### Soldering Component to Board

If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab down to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

### Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 11.8V and set the input supply's current limit to zero. With the input supply off connect up the input supply to  $V_{in}$  and GND. Connect a digital volt meter and a load if needed to set the minimum load of the design from  $V_{out}$  and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.

### Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between  $V_{in}$  and GND, a load is connected between  $V_{out}$  and GND and a current meter is connected in series between  $V_{out}$  and the load. The load must be able to handle at least rated output power + 50% ( 7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.



### Design Assistance

1. Master key : 897D4615475DFAEC[v1]
2. **TPS56339** Product Folder : <http://www.ti.com/product/TPS56339> : contains the data sheet and other resources.

#### Important Notice and Disclaimer

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with TI products.